

Skills Exploration

Watt's Law Assignment


Name: _____

Mark /24



Calculate the missing values for voltage, current or Watts using Watt's Law ($P = V \times I$)

<p>120V 2A P = _____</p>	<p>120V 120W I = _____</p>
<p>V = _____ 5A P = 100W</p>	<p>120V I = _____ P = 60W</p>
<p>120V 1.5A P = _____</p>	<p>120V I = _____ 60W 120W</p>
<p>120V I = _____ 30W 30W</p>	<p>120V 2A 1A 120W P = _____</p>

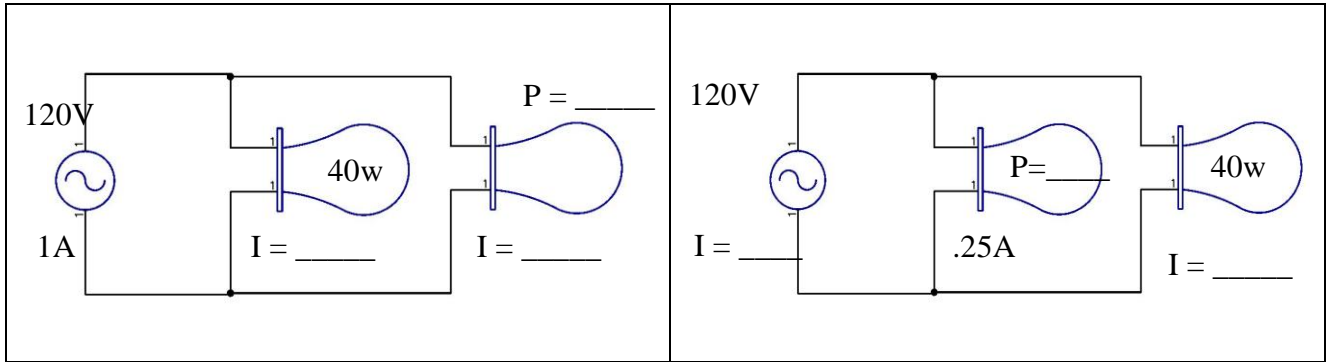

Answer the following Power/Current questions about the different loads in the room. The **Voltage** in the room is **120V**

- 1) What is the maximum current in amps of the Green Mitre Saw?

- 2) What is the maximum current in amps of the Black Table Saw?

- 3) What is the maximum wattage of the microwave. How much current is it drawing?

- 4) What wattage is the heat gun? How many heat guns could be on a circuit before they trip a 15amp?

- 5) What is the maximum output of a laptop power supply in Watts and amps?

- 6) The florescent lights in the room are 30watts each. When all the lights are on, what is the total wattage of them all and what is the total current being used?